




## Experiment (3) Report



Names	IDs	Department	Attendance slot	Group No.	Group Code Part A, B
Adham Alaa Abd Alraheem	2200102	CSE	From 11:00- 13:30 First Rotation	Team 2	A, 13.5

## Part A:

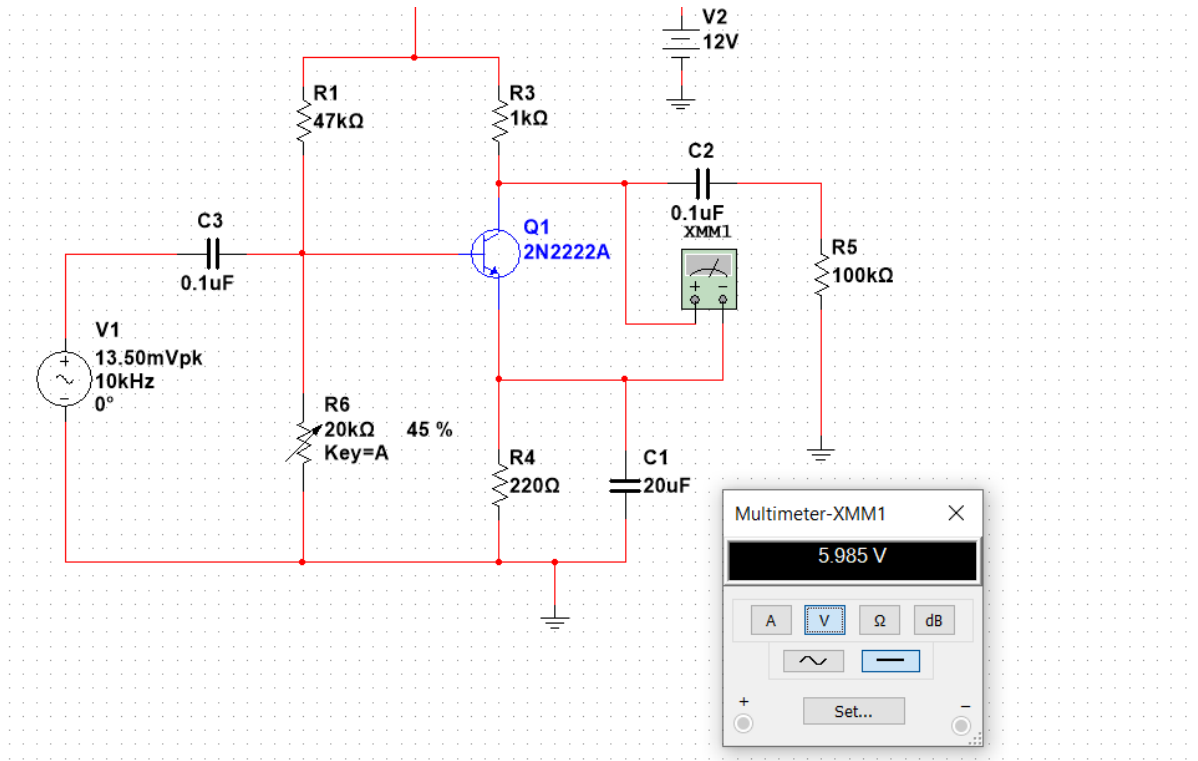
1. The schematic of the circuit drawn in circuit simulator (Figure 1). Adjust the input amplitude to x mV (1 Mark).
2. Tune the circuit till  $V_{CE} \sim V_{CC}/2$ . Report the DC value of  $V_{CE}$  through a snapshot (1 Mark).



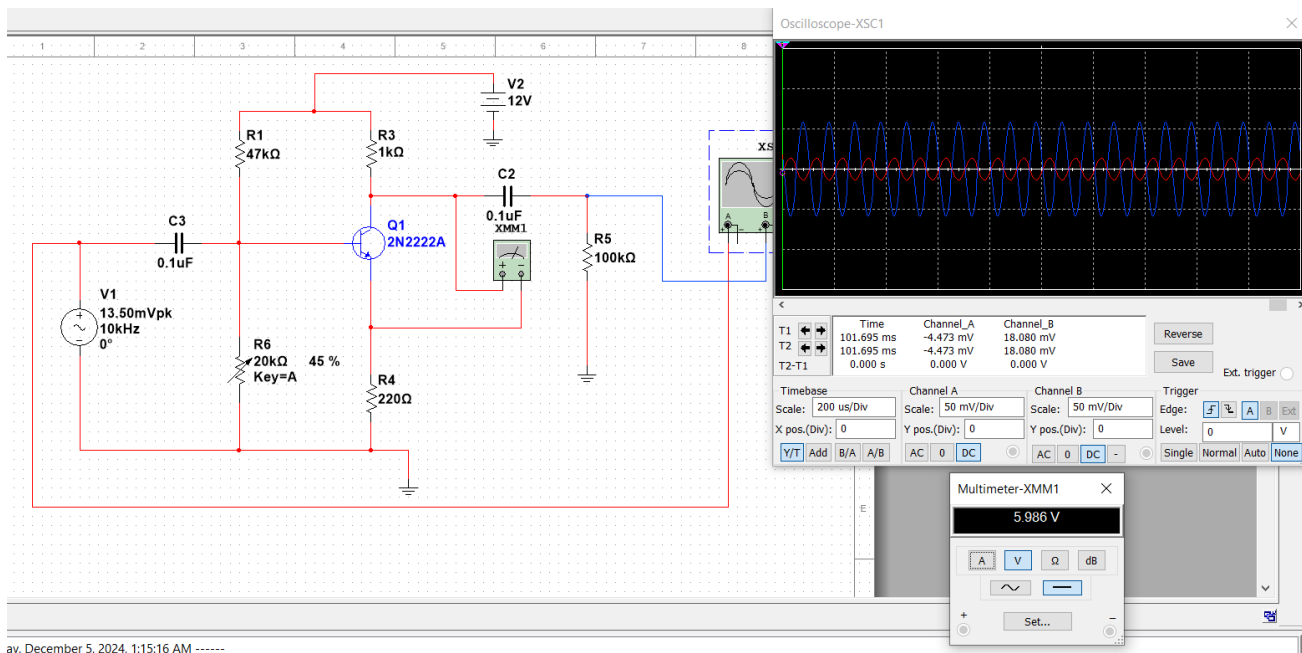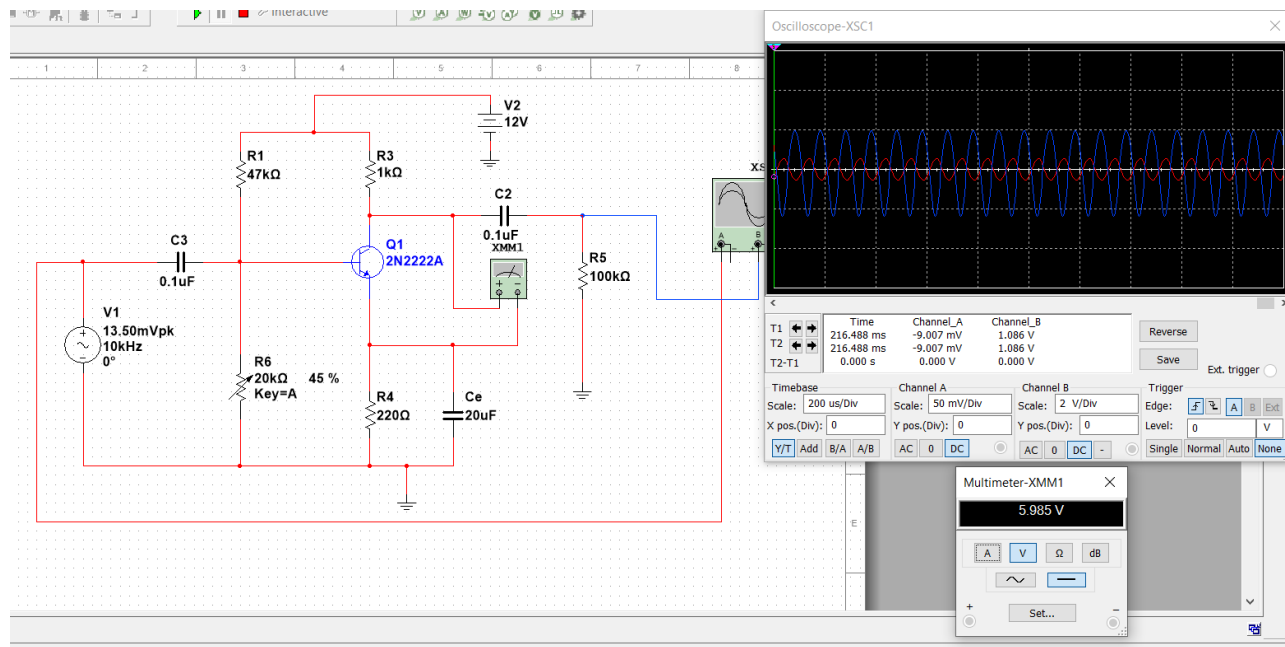
3. Snapshot for the input and the output waveforms, with  $C_e$  connected, another snapshot without  $C_e$  Connected. (1Mark)



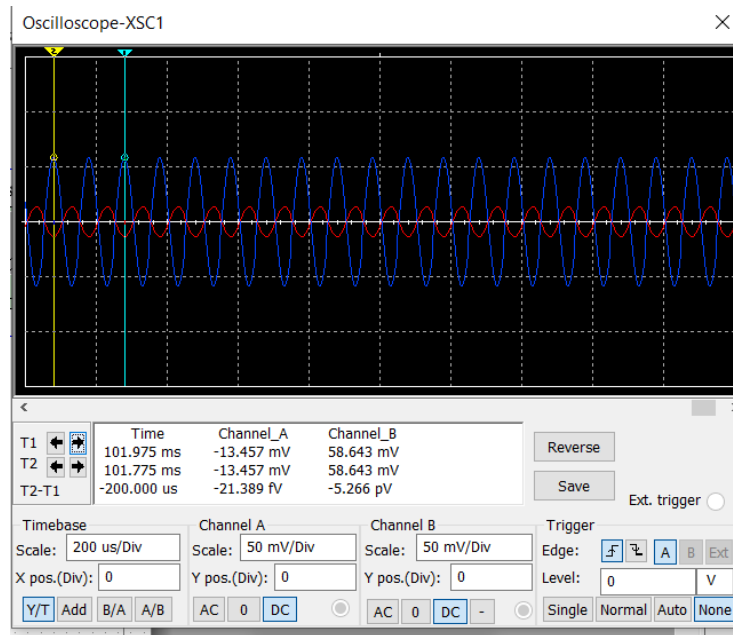4. Measure the gain from simulation results in (3) (1 Mark).



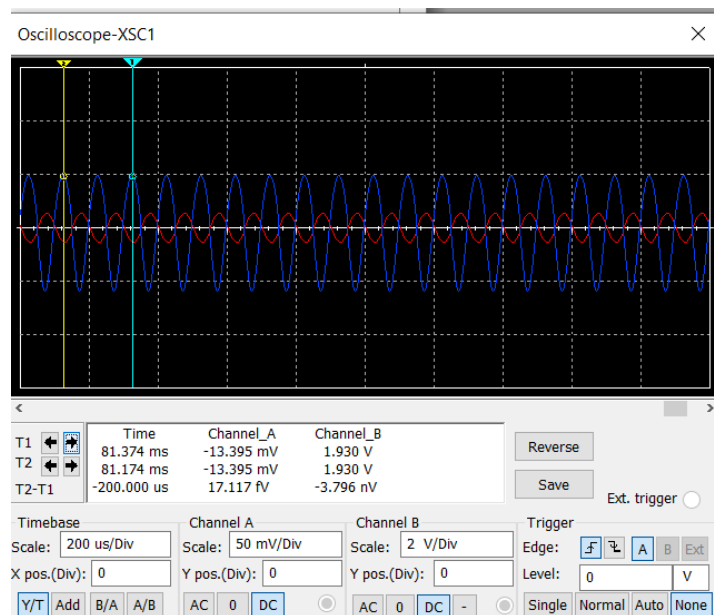Without  $C_e$ , Gain =  $V_{out}/V_{in} = 58.643/-13.457 = -4.36$



With  $C_e$ , Gain =  $V_{out}/V_{in} = 1.930/-13.395 \times 10^{-3} = -144.1$

5. Using hand analysis calculate the analytical gain of this circuit, then compare with the simulation results obtained from measurements in (4). (1 Mark).

$I_{CQ} = 4.33\text{mA}$ ,  $g_m = I_{CQ}/26\text{mV} = 0.165$ , gain =  $g_m * R_c = 165$