




Experiment (4) Report

Names	IDs	Department	Attendance slot	Group No.	Group Code Part A, B
Adham Alaa Abd Alraheem	2200102	CSE	From 11:00-13:30 First Rotation	Team 2	B, 99

Part B:

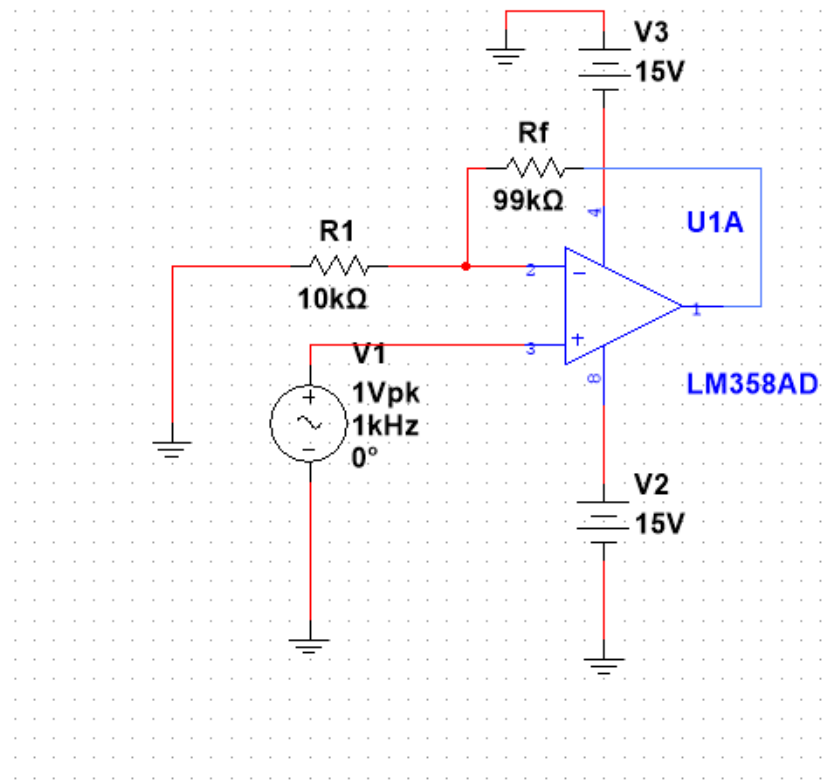
1. The schematic of the circuit of Figure 19.

Adjust the resistance (R1) to 10 K Ω , the Resistance (RF) to x K Ω and supply voltage to $\pm 15\text{V}$. (1 Mark).



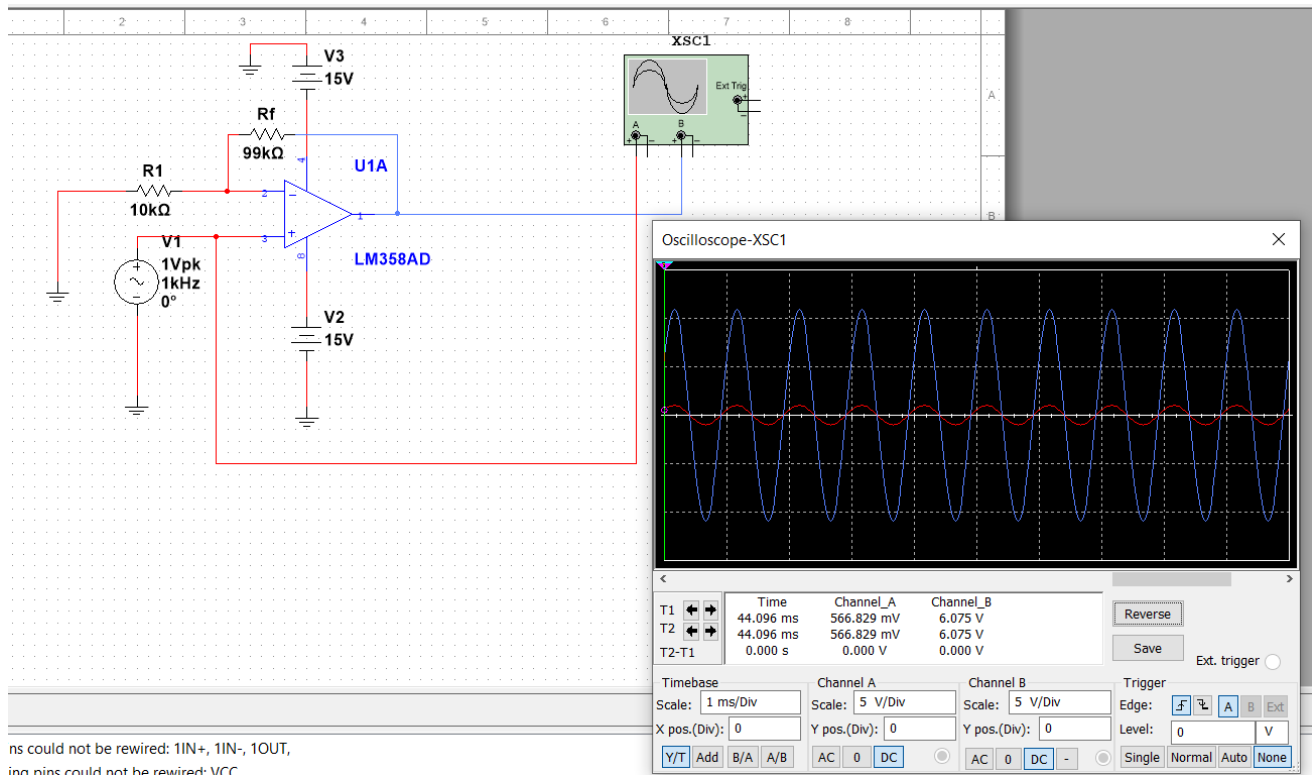2. CRO snapshot displaying input and output waveforms.


(Vin is Sine wave with 1KHz frequency and 2 V-PP). (1 Mark).



3. The voltage gain.


$$V_{out} = V_{in} (1 + R_f/R_1) = 1(1 + 99/10) = 10.9 \text{ V}$$

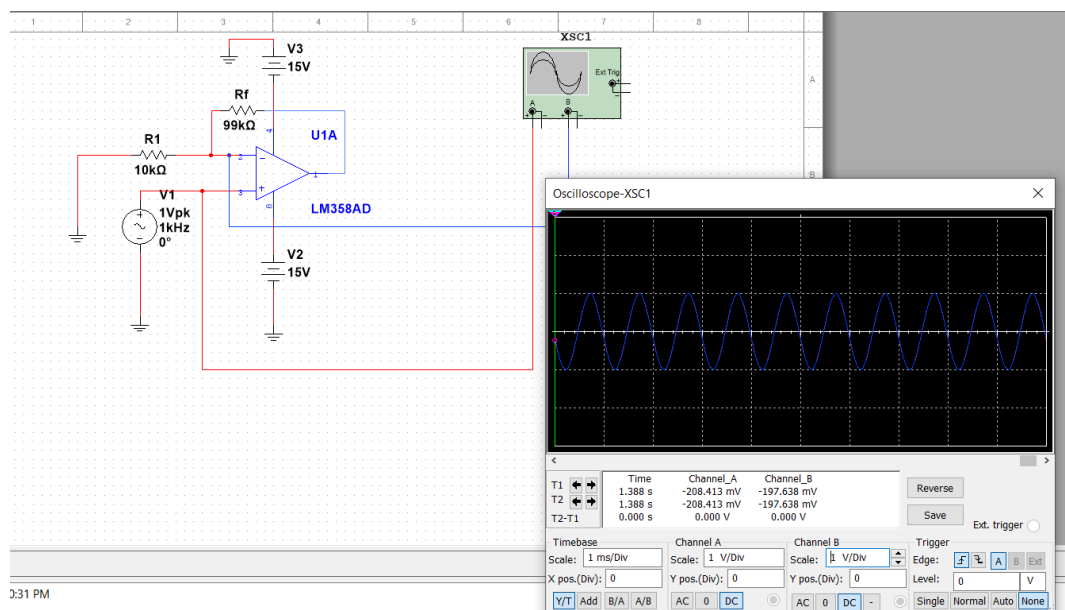4. CRO snapshot displaying the voltage of the negative and positive terminals of the Op-Amp.



The voltage at both terminals is equal

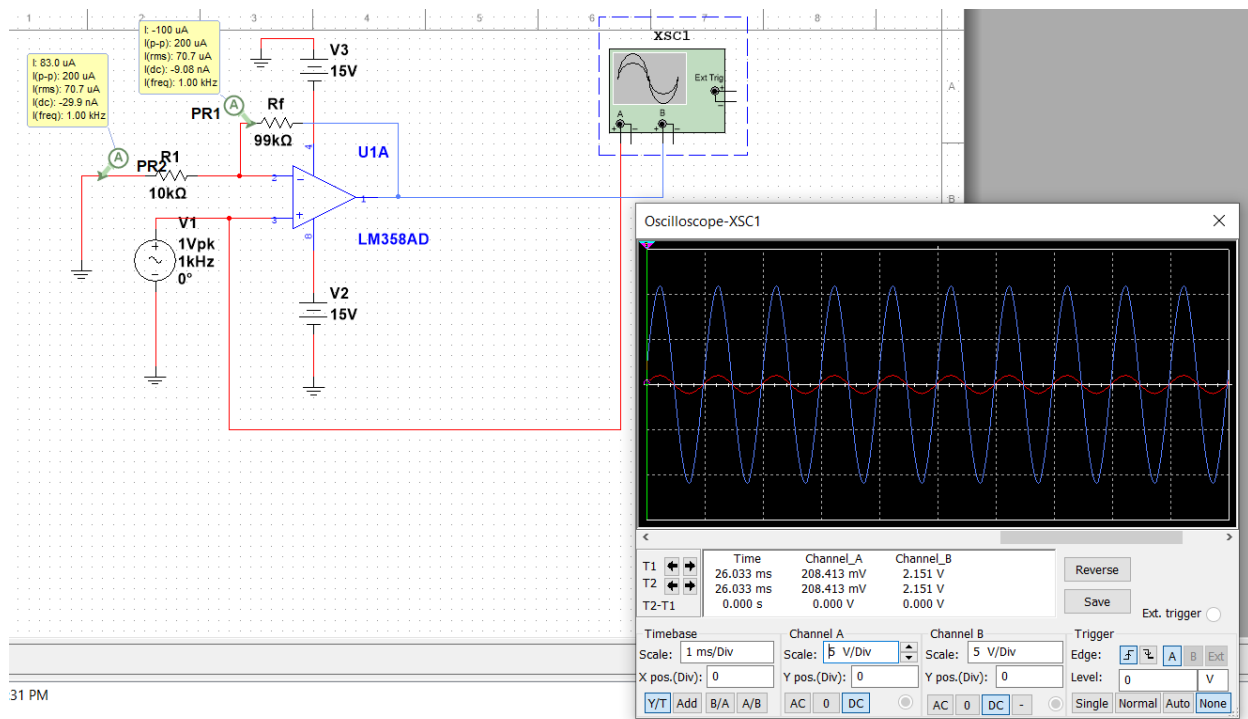5. CRO snapshot displaying current waveforms in the resistors R1 and Rf and compare them to the expected values.



Expected :

$$I_{Rf} = (10.9/V2 - 1/V2)/99000 = 70.71 \text{ uA (rms)}$$

$$I_{R1} = (1/V2)/10000 = 70.71 \text{ uA (rms)}$$